

## Errata

**Document Title:** Reducing The Insertion Loss Of A Shunt PIN Diode (AN 957-2)

**Part Number:** 5952-0491

**Revision Date:** November 1974

---

### HP References in this Application Note

This application note may contain references to HP or Hewlett-Packard. Please note that Hewlett-Packard's former test and measurement, semiconductor products and chemical analysis businesses are now part of Agilent Technologies. We have made no changes to this application note copy. The HP XXXX referred to in this document is now the Agilent XXXX. For example, model number HP8648A is now model number Agilent 8648A.

### About this Application Note

We've added this application note to the Agilent website in an effort to help you support your product. This manual provides the best information we could find. It may be incomplete or contain dated information, and the scan quality may not be ideal. If we find a better copy in the future, we will add it to the Agilent website.

### Support for Your Product

Agilent no longer sells or supports this product. You will find any other available product information on the Agilent website:

[www.agilent.com](http://www.agilent.com)

Search for the model number of this product, and the resulting product page will guide you to any available information. Our service centers may be able to perform calibration if no repair parts are needed, but no other support from Agilent is available.

---

# Reducing the Insertion Loss of a Shunt PIN Diode

## Application Note 957-2

---

A shunt PIN diode is often used as a switch or attenuator. The upper frequency limitation is determined by the increase in insertion loss as the diode capacitance starts to short out the load. Figure 1 shows a symmetrical matching circuit that extends this frequency limitation by incorporating the diode capacitance, C, into a low pass filter. Figure 2 shows the filter response when the inductance value, L, is chosen to form a Chebyshev equal ripple filter.

$$L = R^2C \times g(1) / g(2)$$

The constants  $g(1)$  and  $g(2)$  are low pass prototype element values, available in the literature [1,2] as a function of the ripple value shown in Figure 2. This filter is designed to operate between equal generator and load resistances, R.


The cutoff frequency,  $f_c$ , shown in Figure 2, is determined by the diode capacitance, the ripple value, and R.

$$f_c = g(2) / 2\pi RC$$


For convenience in design, inductance and cutoff frequency are plotted in Figure 3 in terms of VSWR and in Figure 4 in terms of insertion loss. For example, the HP 5082-0001 PIN diode has a zero bias capacitance of 0.18 pF. If a cutoff frequency of 16 GHz is desired, the insertion loss ripple will be 0.007 dB and the VSWR ripple will be 1.072, corresponding to  $f_c C = 2.88$ . The value of L is 0.28 nH corresponding to

$$L / C = 1.54$$


Higher cutoff frequencies or lower ripple may be obtained by lowering the diode capacitance with reverse bias. The capacitance of the 5082-0001 PIN diode is reduced to 0.12 pF with a reverse bias of 20 volts. This increases the cutoff frequency for the same ripple to 24 GHz.

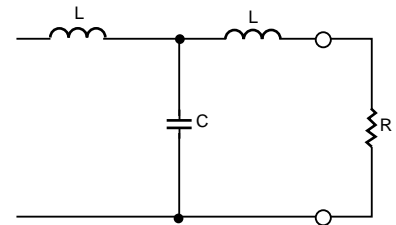


**Figure 1. Low Pass Matching Circuit**

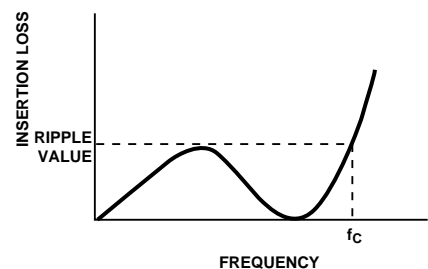

**Figure 2. Chebyshev Response**

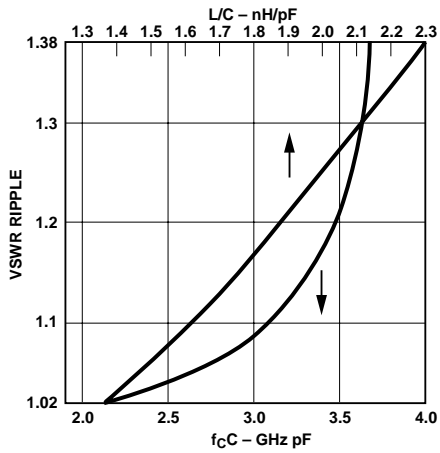

**Figure 3. Filter Design Curves**

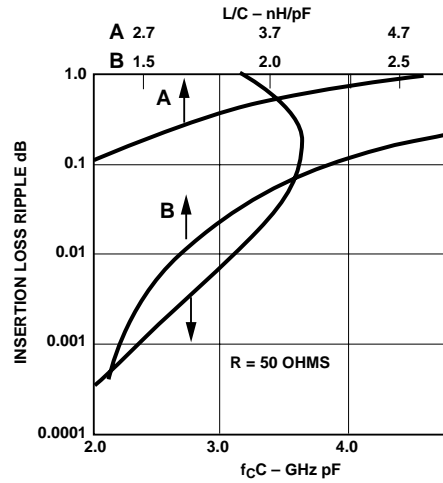

**Figure 4. Filter Design Curves**

**References**

1. L. Weinberg, "Network Analysis and Synthesis", McGraw-Hill, 1962.
2. N. Chitre and M. O'Donovan, "A Unified Design Chart for Small VSWR Filters", Microwave Journal, April 1967, pp 79-84.

For technical assistance or the location of your nearest Hewlett-Packard sales office, distributor or representative call:

**Americas/Canada:** 1-800-235-0312 or (408) 654-8675

**Far East/Australasia:** Call your local HP sales office.

**Japan:** (81 3) 3335-8152

**Europe:** Call your local HP sales office.

Data Subject to Change

Copyright © 1974 Hewlett-Packard Co.

Printed in U.S.A. 5952-0491 (11/74)